

High-Voltage Pulse Transient Safety Design for bq243xx

Mao Ye

PMP - Portable Power

ABSTRACT

The maximum input voltage rating of the bq243xx family of ICs is 30 V. However, some customers like to do high-voltage pulse transient test to prove its high-voltage capability and reliability from a system level. This pulse transient voltage could be as high as 45 V with 1-A output current limit and 200- μ s pulse width. It is important for system designers to properly design the charging system with correct system-level protections. Usually, a varistor or Zener diode is used for clamping such high-pulse transient voltage so that the maximum input voltage from the bq243xx is less than the absolute maximum voltage of 30 V for safe operation.

1 Test Setup

Figure 1 shows the high-voltage transient test schematic. A 1- μ F input capacitor and a 1- μ F output capacitor are used for charging front-end bq243xx devices. A 1-k Ω resistor, R4, is used to discharge high voltage after 200 μ s so that subsequent testing can be performed; otherwise, a high voltage remains at the input, delaying further testing. This resistor is not required in real applications. A function generator is used to generate a 5-V, 200- μ s control signal to trigger the high-voltage amplifier.

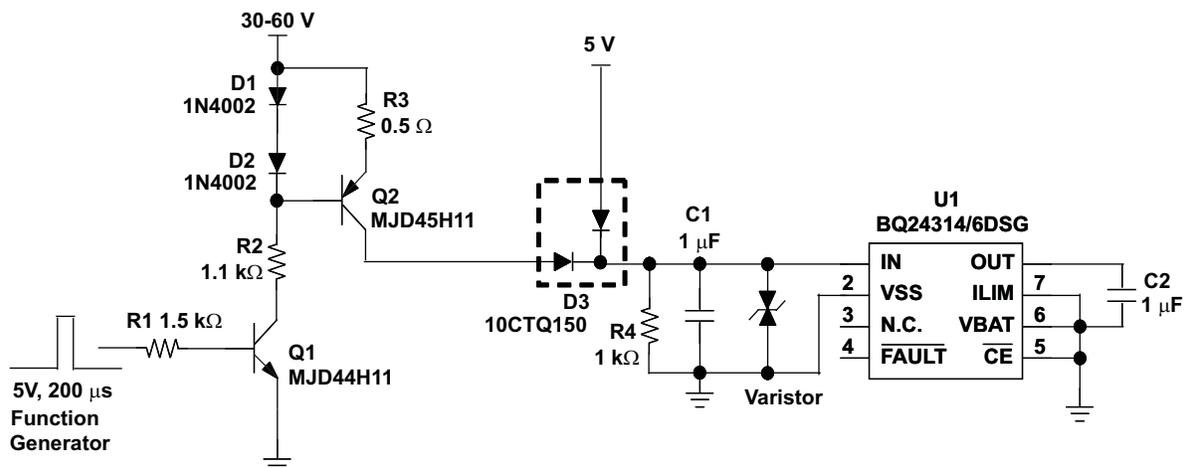


Figure 1. High-Voltage Pulse Transient Test Schematic

In the following test waveforms, CH1, CH2, CH3, and CH4 are represented as follows:

CH1: control signal, 5 V/div

CH2: IN pin, 10 V/div

CH3: OUT pin, 5 V/div

CH4: input current, measured before input capacitor, 1 A/div.

Test Setup

1.1 Test One: Varistor Type One

In test 1, a 2012002931W_MLVS-0402-M07 20A 9V 0402_Inpaq varistor is used. The test results are shown in the following illustrations. The high voltage is set from 30 V to 60 V with a 5-V step.

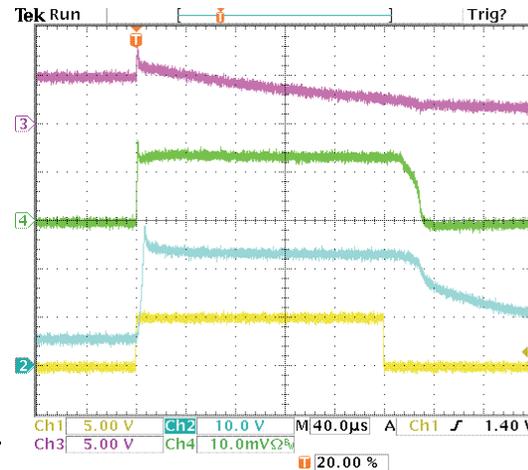
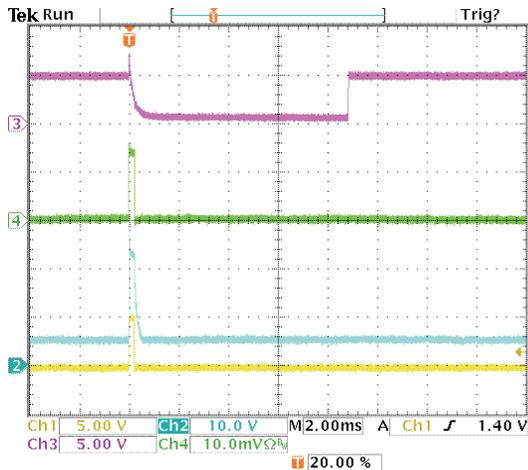


Figure 2. Vin From 5 V to 30 V

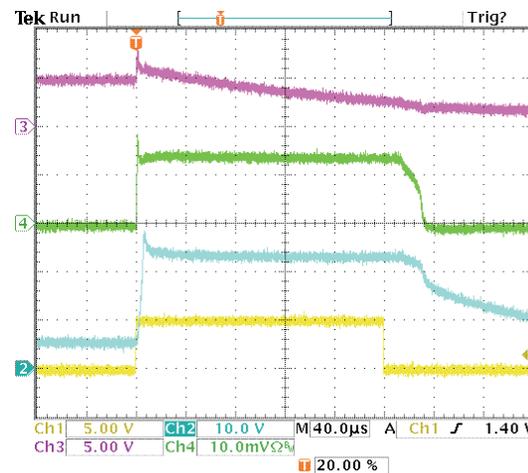
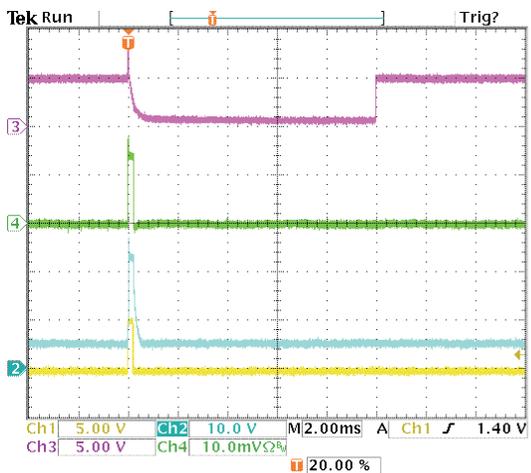


Figure 3. Vin From 5 V to 35 V

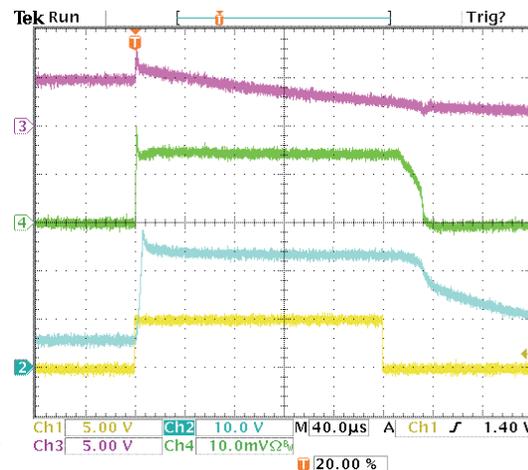
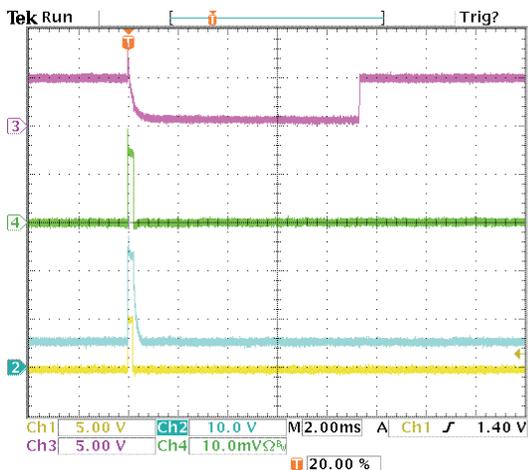


Figure 4. Vin From 5 V to 40 V

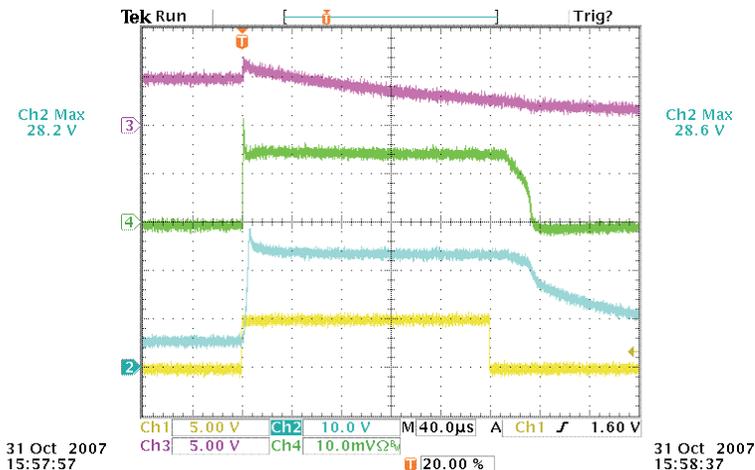
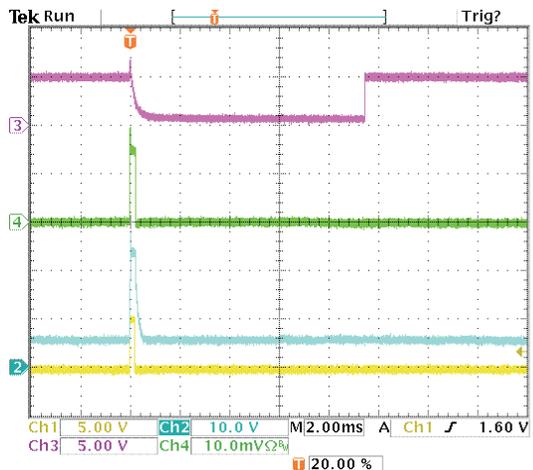


Figure 5. Vin From 5 V to 45 V

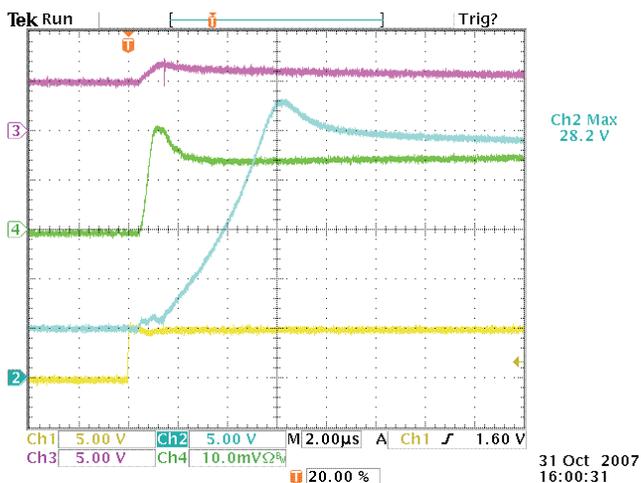


Figure 6. Vin From 5 V to 45 V, 2-μs Time Scale Zoom in Detail, CH2 5 V/div

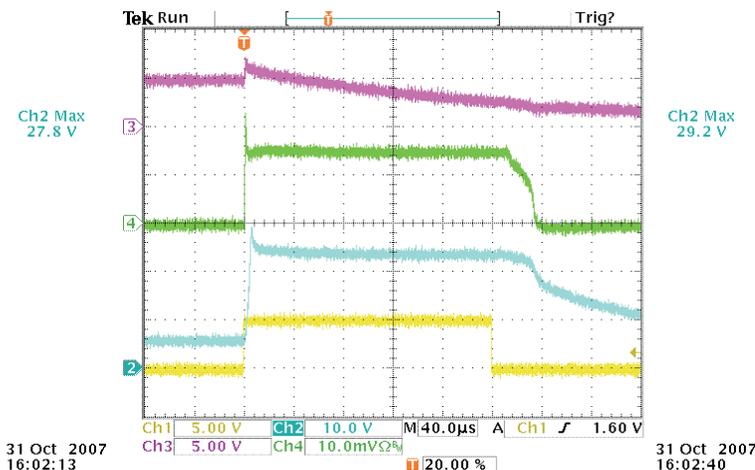
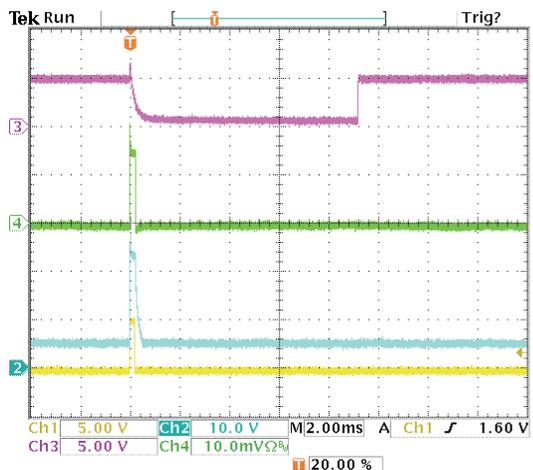


Figure 7. Vin From 5 V to 50 V

Test Setup

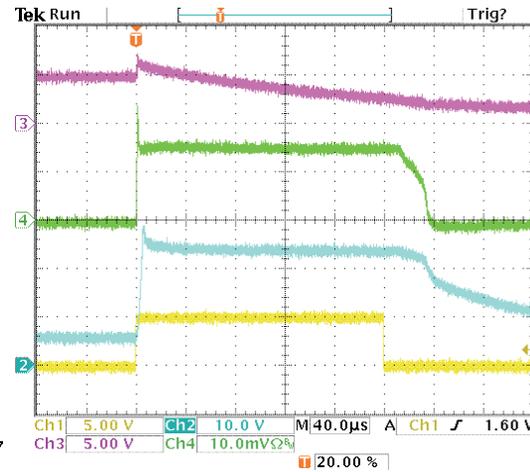
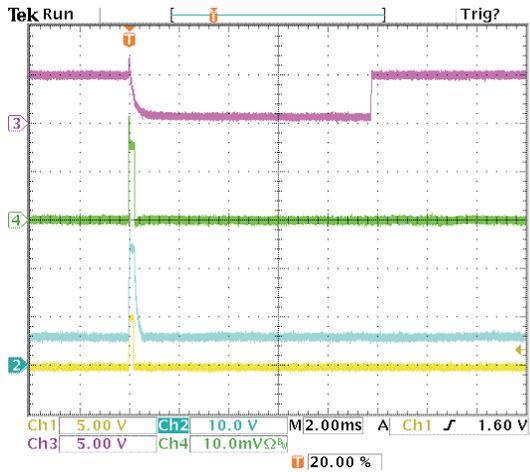


Figure 8. Vin From 5 V to 55 V

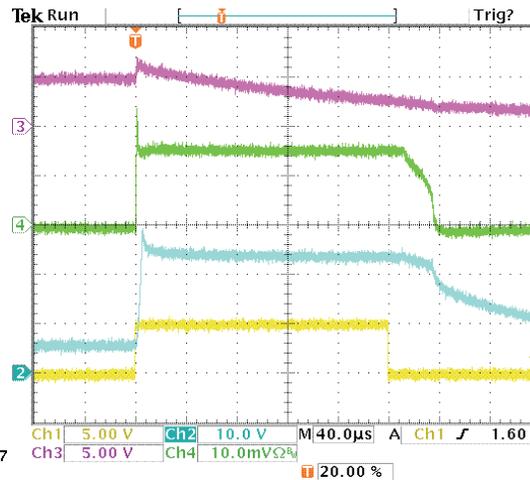
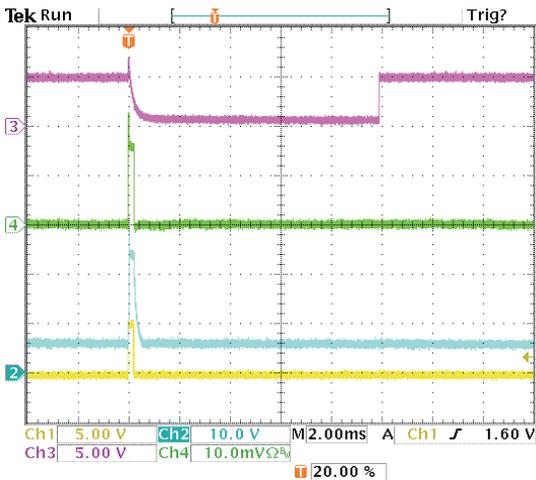


Figure 9. Vin From 5 V to 60 V

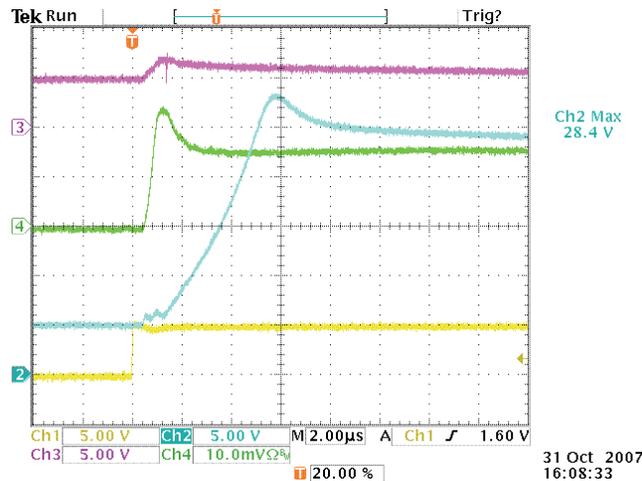


Figure 10. Vin From 5 V to 60 V, 2-μs Time Scale Zoom in Detail, CH2 5 V/div

1.2 Test Case 2: Varistor Type 2

In test 2, 2010000931W_TVM0G090M201R_Thinking is used. The test results are shown in the following illustrations. The high voltage is set from 30 V to 60 V.

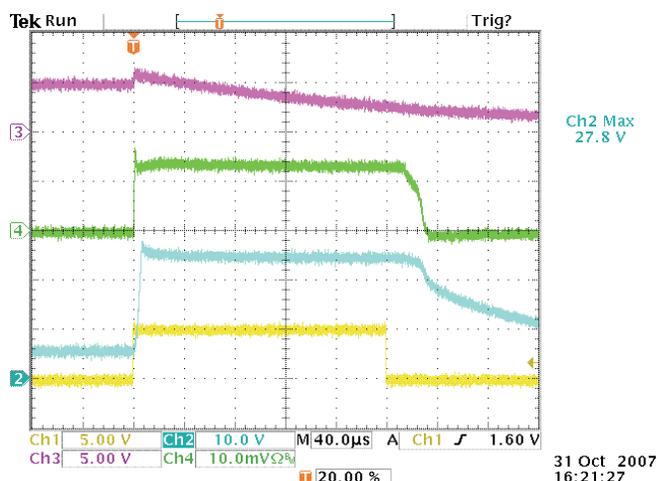
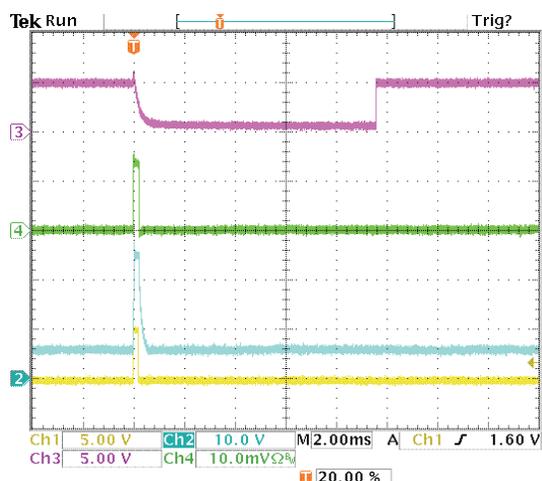


Figure 11. Vin From 5 V to 30 V

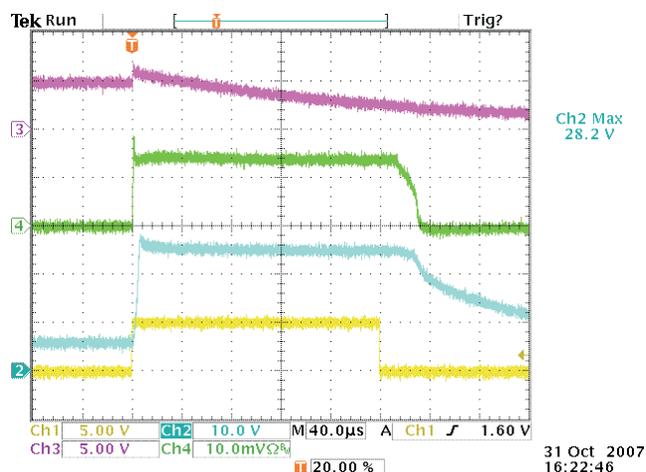
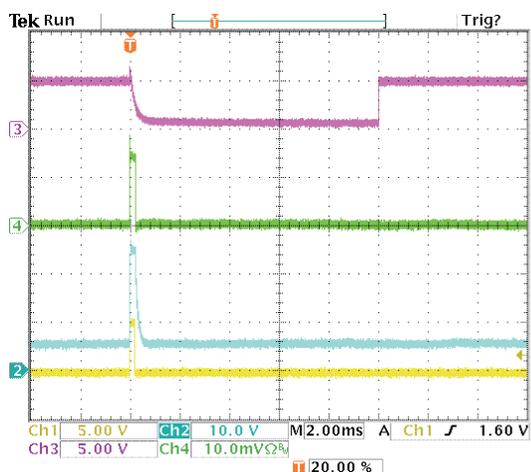


Figure 12. Vin From 5 V to 35 V

Test Setup

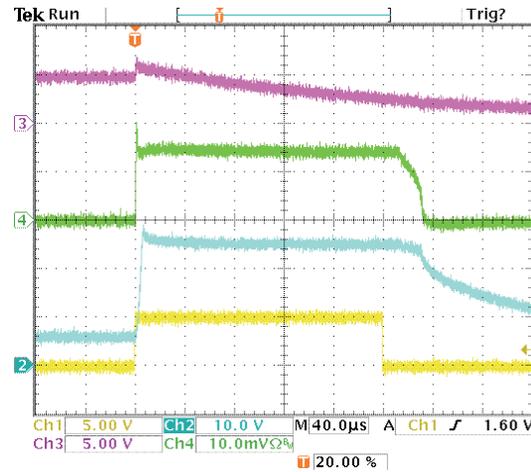
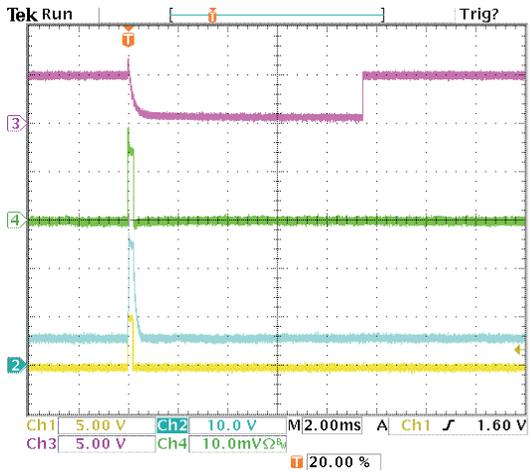


Figure 13. Vin From 5 V to 40 V

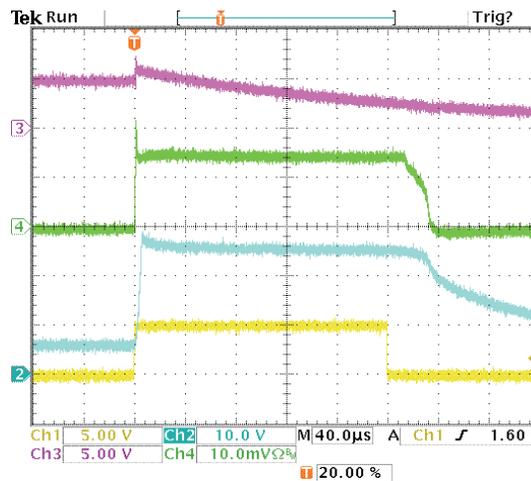
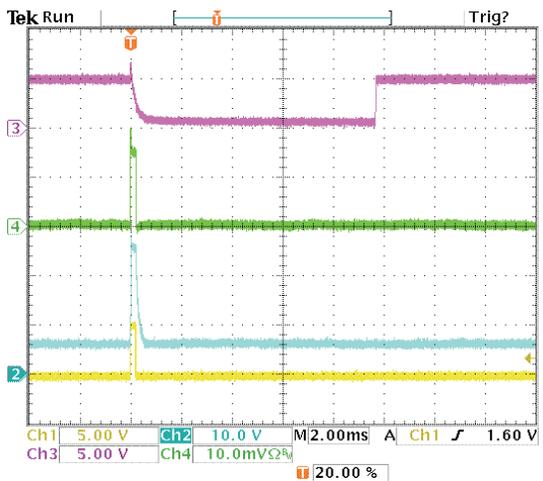


Figure 14. Vin From 5 V to 45 V



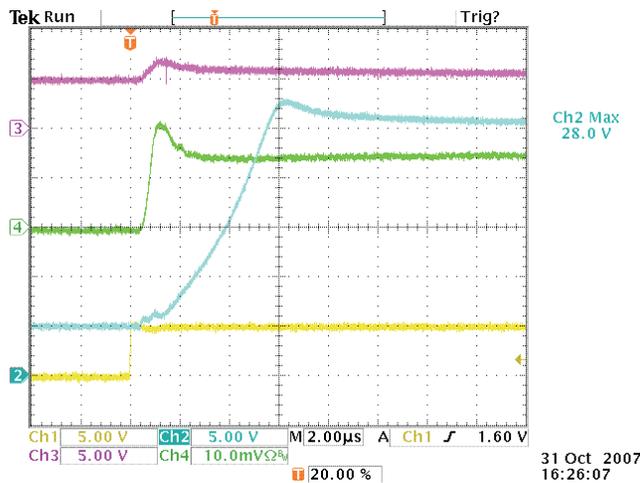


Figure 15. Vin From 5 V to 45 V, 2-μs Time Scale Zoom in Detail, CH2 5 V/div

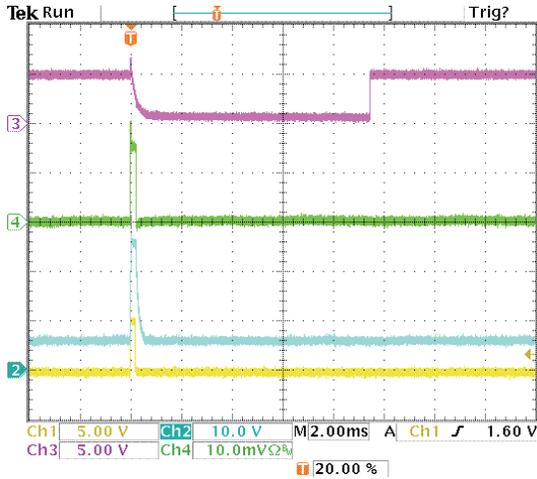


31 Oct 2007 16:27:16

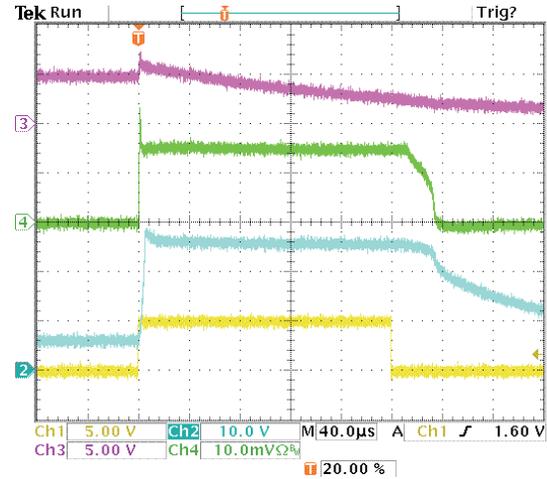


31 Oct 2007 16:27:47

Figure 16. Vin From 5 V to 50 V

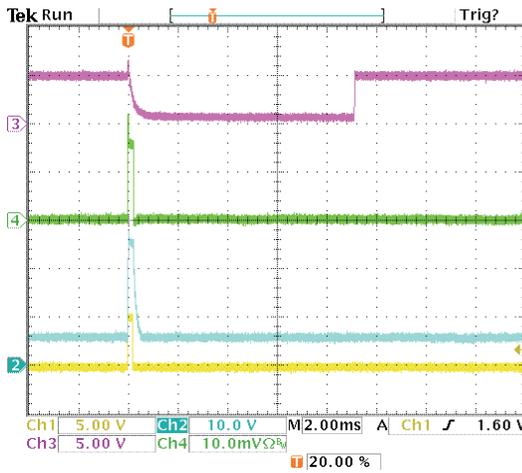


31 Oct 2007 16:28:35

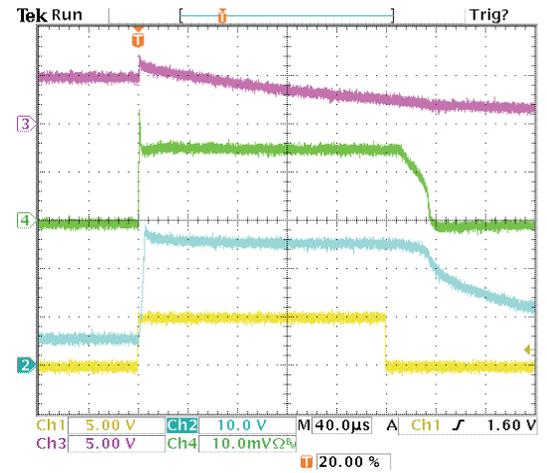


31 Oct 2007 16:29:12

Figure 17. Vin From 5 V to 55 V

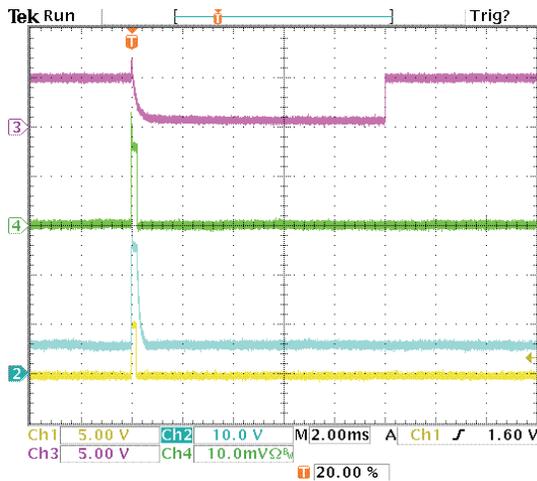

31 Oct 2007 16:30:14

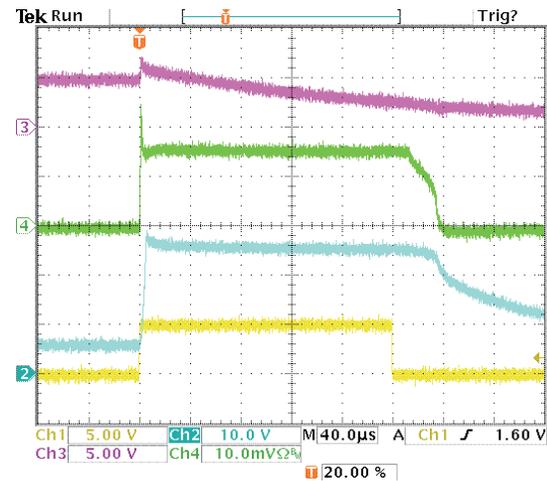

31 Oct 2007 16:30:42

Figure 18. Vin From 5 V to 60 V

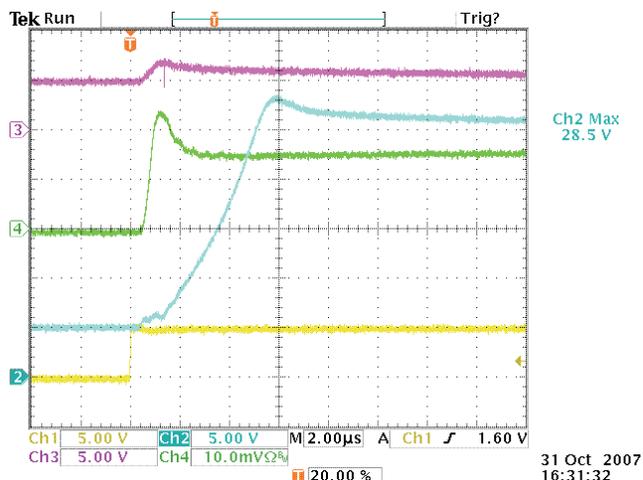


Figure 19. Vin From 5 V to 60 V, 2- μ s Time Scale Zoom in Detail, CH2 5 V/div

The clamping voltage across the varistor or Zener diode is determined by the current flowing into the varistor or Zener diode. The higher the current flowing into the varistor or Zener diode, the higher the clamping voltage. Properly selecting the varistor and Zener diode is critical. The maximum voltage across the bq243xx under these high-voltage transients is determined by the clamping voltage of the varistor or Zener diode.

2 Conclusion

Both varistors can clamp voltage to below 30 V. The clamping voltage is 28.2 V and 28 V for type-one and type-two varistors with 45-V input transient. Even with 60-V input transient, the maximum clamping voltage is 28.4 V and 28.5 V, respectively. The 30-V bq243xx is safe under this kind of voltage level.

In summary, bq243xx passes the 45-V/1- A/200- μ s pulse transient test with the setup shown in [Figure 1](#) using the recommended varistor.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated